

Sayısal Devre Simülatörü


2009 - Samsun

Backward

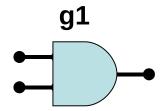


```
>>> g1 = AndGate("G1")
```

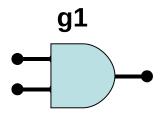


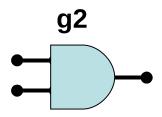


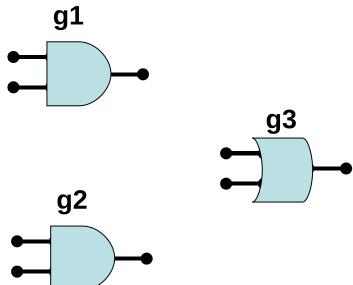
```
>>> g1 = AndGate("G1")
>>> g2 = AndGate("G2")
```



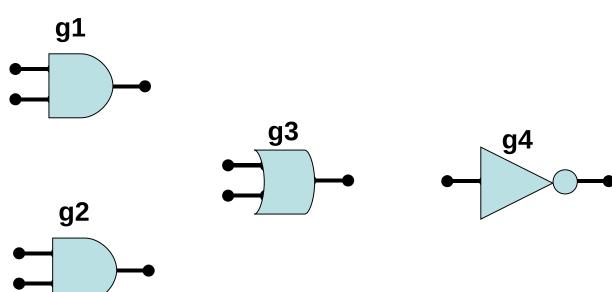
```
>>> g1 = AndGate("G1")
>>> g2 = AndGate("G2")
>>> g3 = OrGate("G3")
```




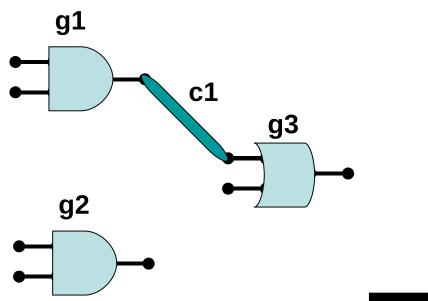

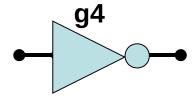

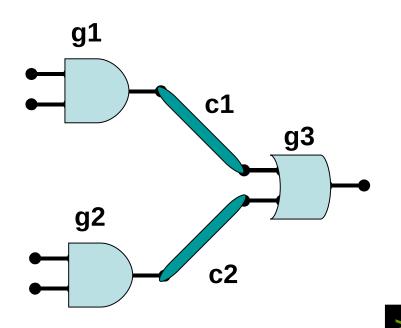
```
>>> g1 = AndGate("G1")
>>> g2 = AndGate("G2")
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
```




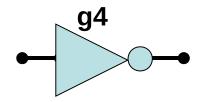

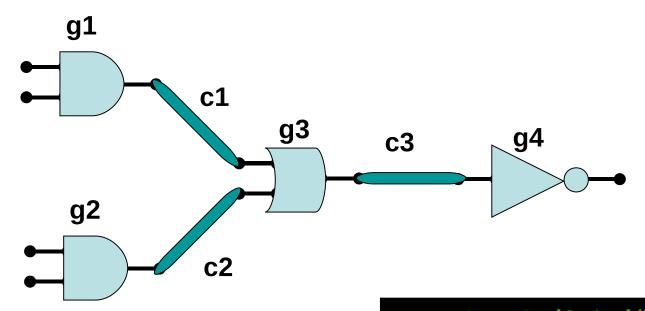
```
>>> g1 = AndGate("G1")
>>> g2 = AndGate("G2")
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
>>> c2 = Connector(g2, g3)
```


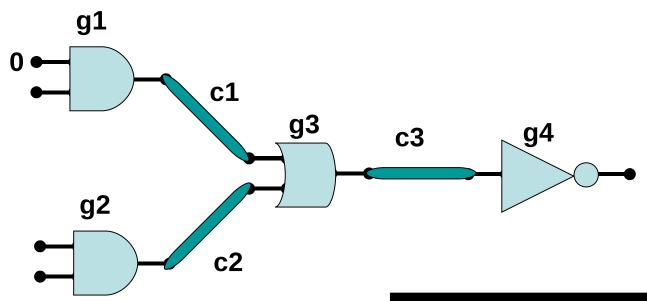
```
>>> g1 = AndGate("G1")
>>> g2 = AndGate("G2")
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
>>> c2 = Connector(g2, g3)
>>> c3 = Connector(g3, g4)
```




G1→PinA: 0

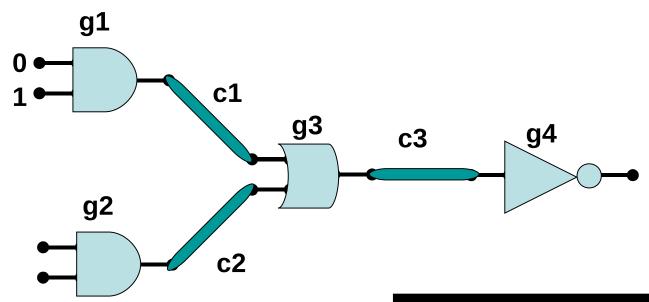

G1→PinA: 0


G1→PinB: 1

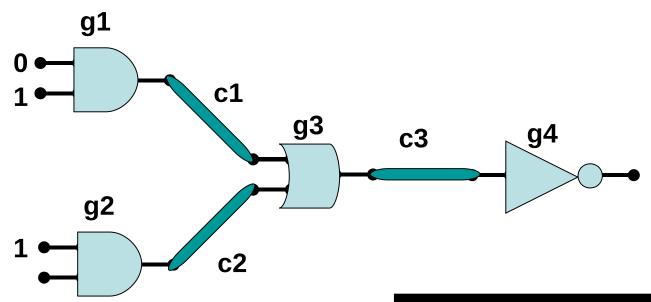

G1→PinA: 0

G1→PinB: 1


G2→PinA: 1

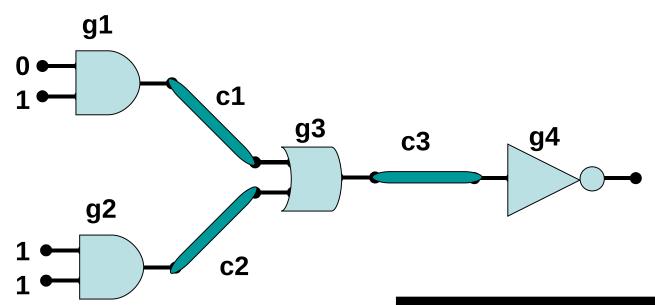

G1→PinA: 0

G1→PinB: 1


G2→PinA: 1

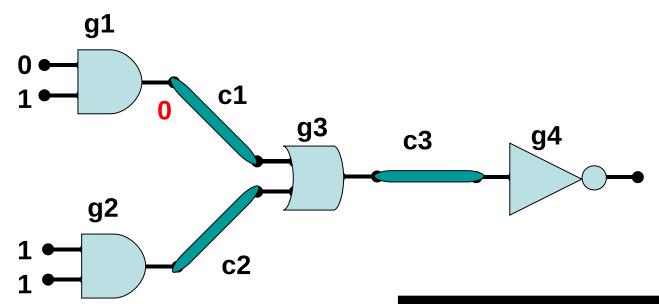

G1→PinA: 0

G1→PinB: 1


G2→PinA: 1

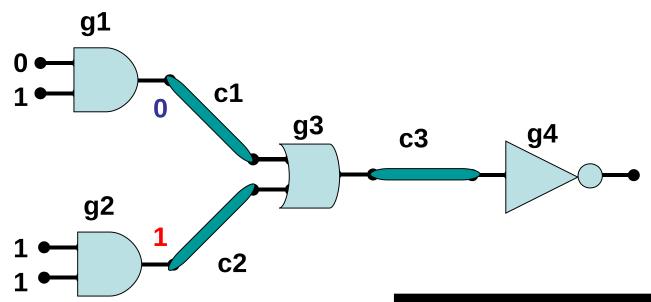

G1→PinA: 0

G1→PinB: 1


G2→PinA: 1

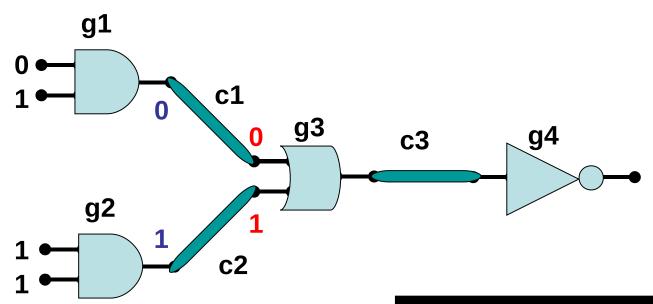

G1→PinA: 0

G1→PinB: 1


G2→PinA: 1

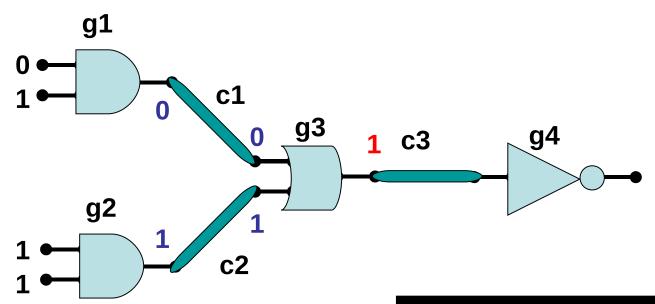

G1→PinA: 0

G1→PinB: 1


G2→PinA: 1

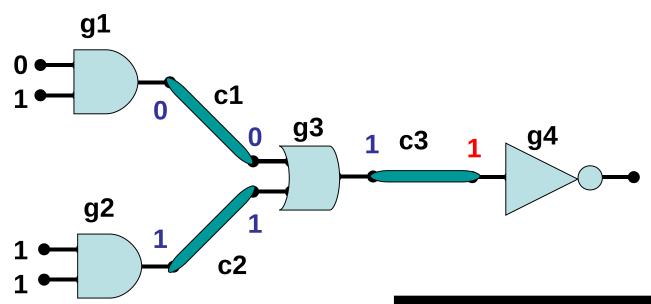

G1→PinA: 0

G1→PinB: 1

G2→PinA: 1

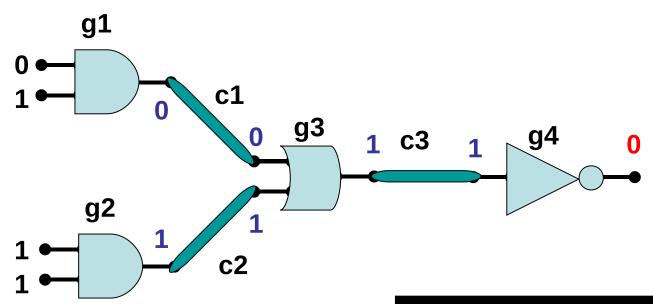

```
>>> g4.getOutput()
```

G1→PinA: 0


G1→PinB: 1

G2→PinA: 1


G2→PinB: 1


0

Forward

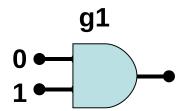


```
>>> g1 = AndGate("G1",0,1)
```

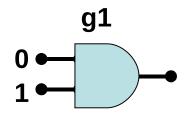


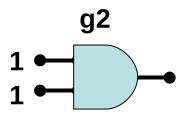

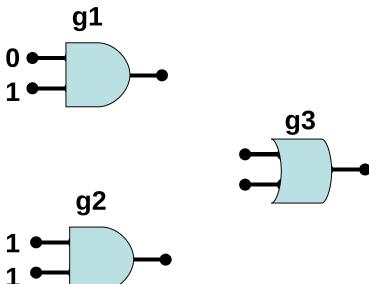
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
```



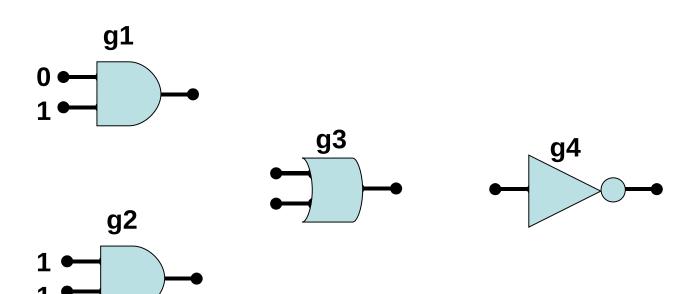
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
```




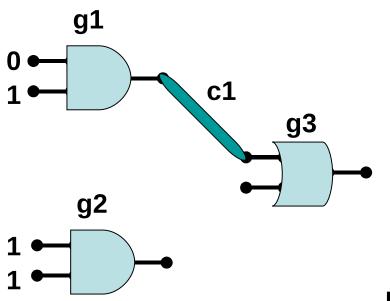
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")



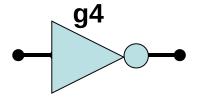


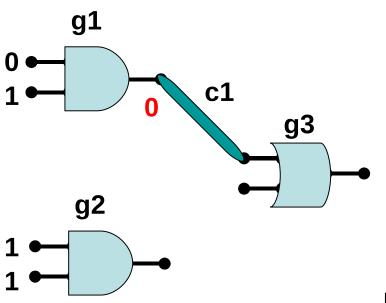
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
```



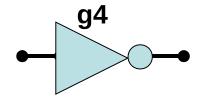


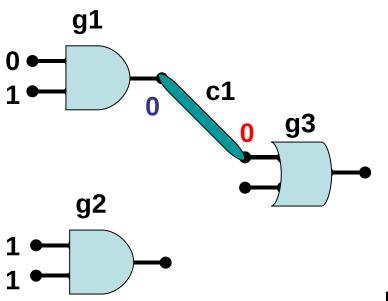
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
```



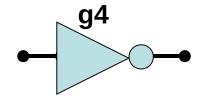

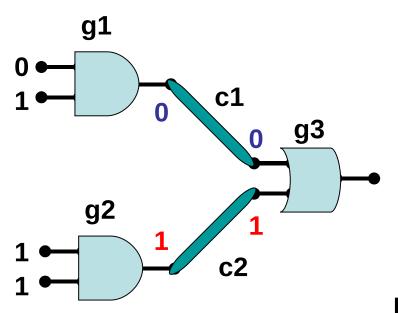
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
```




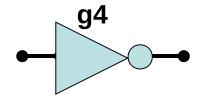
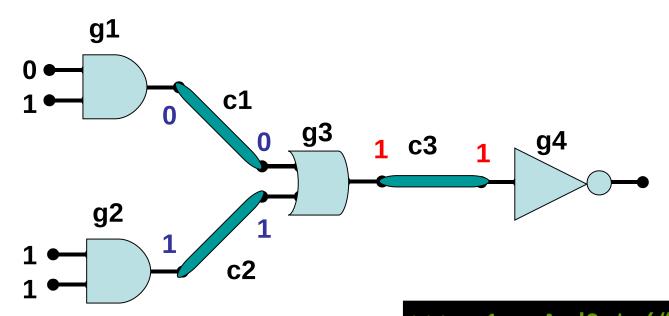
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
>>> c2 = Connector(g2, g3)
```


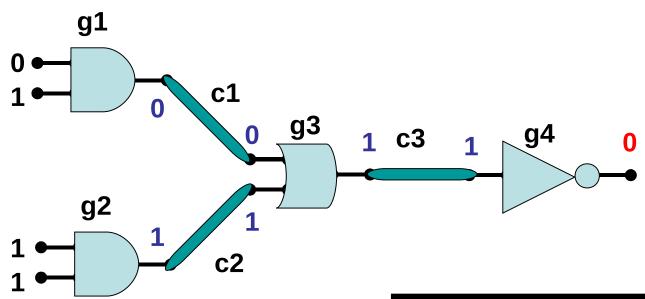
```
>>> g1 = AndGate("G1",0,1)
>>> g2 = AndGate("G2",1,1)
>>> g3 = OrGate("G3")
>>> g4 = NotGate("G4")
>>> c1 = Connector(g1, g3)
>>> c2 = Connector(g2, g3)
>>> c3 = Connector(g3, g4)
```



0